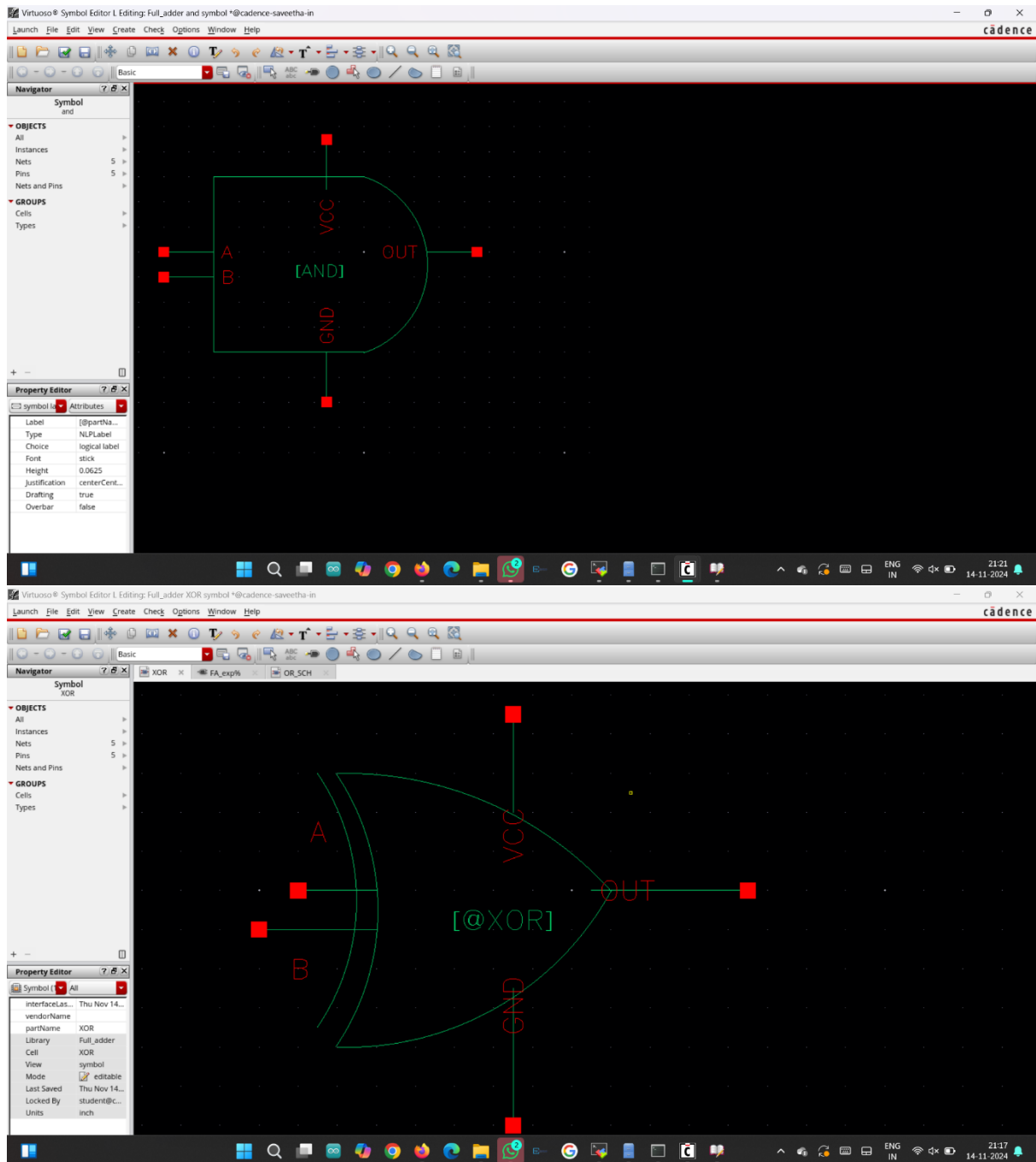


FULL ADDER

AND GATE & XOR GATE



FULL ADDER

SCHEMATIC AND OUTPUT

